



University
of Glasgow

HIGH FREQUENCY COMMUNICATION SYSTEMS

Lecture 4

Hasan T Abbas & Qammer H Abbasi

Spring 2022

- Transmission Lines Theory & Analysis
- Load Mismatching
- The Magic of Quarter-wave Transformer

THE TRANSMISSION LINES

- A technique to bridge the gap between basic circuit analysis and electromagnetic fields theory
 - Lots of similarities and analogies
- Commonly used to design microwave devices and circuits
- We use transmission lines when the electrical length of the device is greater than $\lambda/10$.

- In wave scattering problems, we place the co-ordinate system at the boundary
- In transmission lines, we use the two different lines as the boundary
- For open problems, the load is considered to be at infinity.


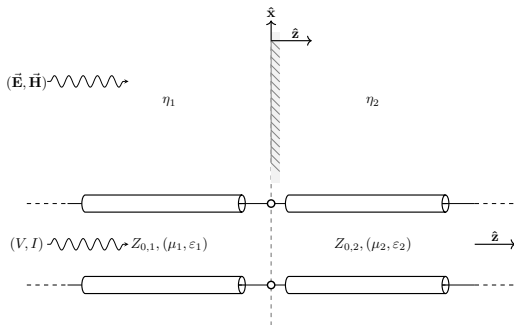
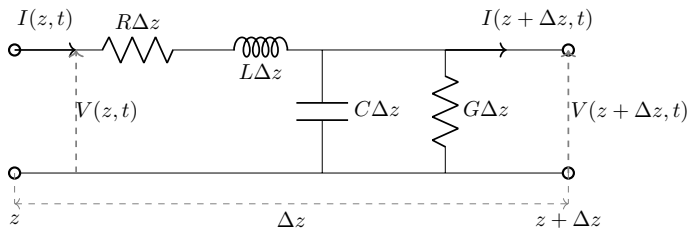


Figure 1: The analogy between wave problems and transmission lines.

TL Theory	EM Field Theory
$V_1 = V_0 e^{-j\gamma_1 z} (1 + \Gamma_L e^{j2\gamma_1 z})$	$E_{x,1} = E_0 e^{-jk_1 z} (1 + \Gamma e^{j2k_1 z})$
$I_1 = \frac{V_0}{Z_{0,1}} e^{-j\gamma_1 z} (1 + \Gamma_L e^{j2\gamma_1 z})$	$H_{x,1} = \frac{E_0}{\eta_0} e^{-jk_1 z} (1 + \Gamma e^{j2k_1 z})$
$\Gamma_L = \frac{Z_L - Z_{0,1}}{Z_L + Z_{0,1}} = \frac{Z_{0,2} - Z_{0,1}}{Z_{0,2} + Z_{0,1}}$	$\Gamma = \frac{\eta_2 - \eta_1}{\eta_2 + \eta_1}$
$V_2 = T V_0 e^{-j\gamma_2 z}$	$E_{x,2} = T E_0 e^{-jk_2 z}$
$I_2 = T \frac{V_0}{Z_{0,2}} e^{-j\gamma_2 z}$	$H_{x,2} = T \frac{E_0}{\eta_2} e^{-jk_2 z}$
$T = \frac{2Z_{0,2}}{Z_{0,2} + Z_{0,1}}$	$T = \frac{2\eta_2}{\eta_2 + \eta_1}$

- For a transmission line, we use a distributed circuit approach
 - Energy stored in the magnetic field $\rightarrow L$
 - Energy stored in the electric field $\rightarrow C$
 - Conductive losses $\rightarrow R$
 - Dielectric losses $\rightarrow G$
- All the circuit elements are expressed per unit length
- We can express the voltage and current at any given point z and time t .

THE TRANSMISSION LINE EQUATION

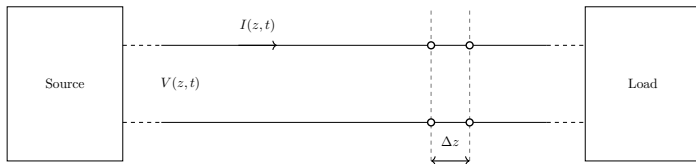

- Solving the electric circuit leads to a second order differential equation
- Analogous to the wave equation
 - Hence the analogies between voltage V and electric field \vec{E}


$$\left\{ \frac{\partial^2}{\partial z^2} - [(R + j\omega L)(G + j\omega C)] \right\} V(z, t) = 0$$

The solution is of the type:

$$V(z) = V_+ e^{-\gamma z} + V_- e^{+\gamma z}$$

where the propagation constant $\gamma = \sqrt{(R + j\omega L)(G + j\omega C)}$. For a lossless case $R = G = 0$.

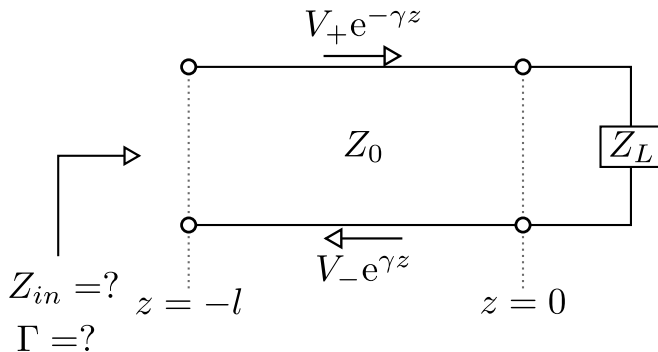- For a transmission line terminated with a load Z_L
 - We get reflections in the line (superposition incoming and reflected wave make up the total voltage)
- The input impedance depends on the Z_L as well as the length l of the transmission line
- For Transmission line analysis, we shift the origin to the load.



The *voltage reflection coefficient* Γ can for the line is

$$\begin{aligned}\Gamma &= \frac{V_{ref}}{V_{inc}} = \frac{V_- e^{\gamma z}}{V_+ e^{-\gamma z}} \\ &= \frac{V_{-,z=0}}{V_{+,z=0}} e^{2\gamma z} = \Gamma_L e^{2\gamma z}\end{aligned}$$

We can express the voltage at any point on the line as:

$$V(z) = V_+ (e^{-\gamma z} + \Gamma_L e^{\gamma z})$$

After finding a similar expression for the current, we can write the impedance as:

$$Z(z) = Z_0 \frac{e^{-\gamma z} + \Gamma_L e^{-\gamma z}}{e^{-\gamma z} - \Gamma_L e^{-\gamma z}}$$

At $z = 0$, $Z(0) = Z_L$, and we get:

$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} \implies \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

At $z = -l$, the input impedance $Z(-l) = Z_{in}$ is given by:

$$\begin{aligned} Z(-l) &= Z_0 \frac{e^{\gamma l} + e^{-\gamma l} \Gamma_L}{e^{\gamma l} - e^{-\gamma l} \Gamma_L} \\ &= Z_0 \frac{(Z_L + Z_0) e^{\gamma l} + (Z_L - Z_0) e^{-\gamma l}}{(Z_L + Z_0) e^{\gamma l} - (Z_L - Z_0) e^{-\gamma l}} \\ &= Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} \end{aligned}$$




For lossless TLs $\gamma = j\beta$, therefore,

$$Z(-l) = Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l}$$

For $Z_L = 0$,

$$Z_{in} = Z_0 j \tan(\beta l)$$




$$\Gamma_{in} = -1$$

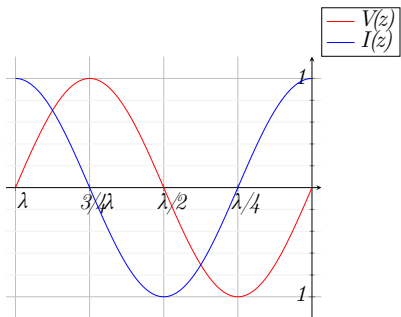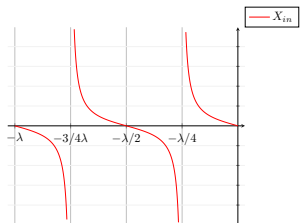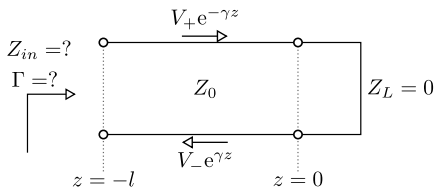

For $Z_L = \infty$,

$$Z_{in} = -Z_0 j \cot(\beta l)$$


$$\Gamma_{in} = 1$$

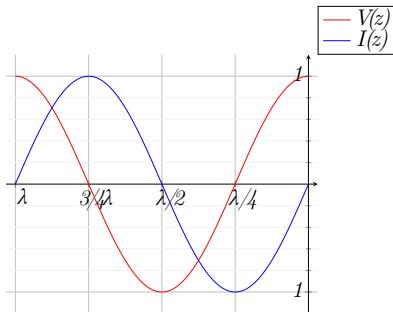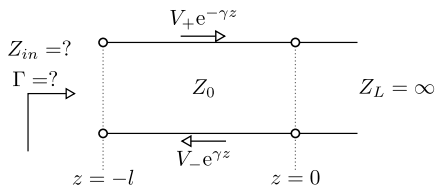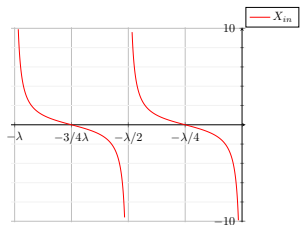

For $Z_L = Z_0$,


$$Z_{in} = Z_0$$

$$\Gamma_{in} = 0$$

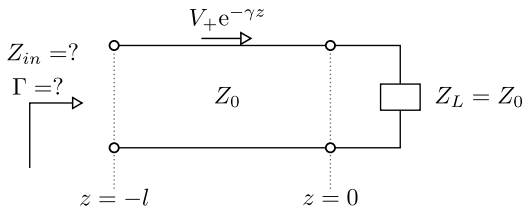

- Ideally we desire this condition for maximum power transfer.
- No reflections take place in this case

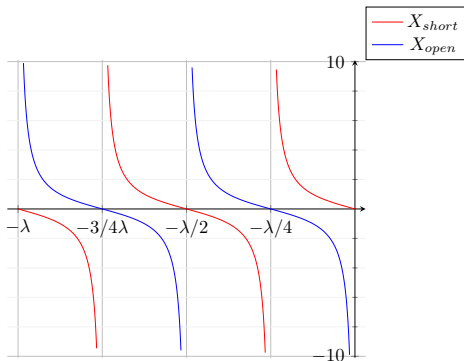- We see that for terminated loads with special lengths that are multiples of quarter wavelengths ($\lambda/4 + n\lambda/2$) for $n = 1, 2, 3, \dots$
- The load impedance is inverted
 - Open-circuit load becomes short-circuit and vice versa
- For such a line, the input impedance is $Z_{in} = \frac{Z_0^2}{Z_L}$



- We want maximum power transferred to the load from the transmission line.
 - For that to happen, we require the impedance matching of the transmission line.
- The reflections in the TL are undesirable and lead to a standing wave generation ($V = V_+ + V_-$).
- The voltage standing wave ratio (VSWR) measures the quality of impedance matching in TL.

Recall,

$$V(z) = V_+ (e^{-\gamma z} + \Gamma e^{\gamma z})$$

The values of the voltage reflection coefficient range from $-1 \leq |\Gamma| \leq 1$.

The VSWR is the ratio of the maximum and minimum absolute values of the voltage

$$VSWR = \frac{|V_{max}|}{|V_{min}|}$$

In other words,

$$|V_{max}| = V_0 (1 + |\Gamma|)$$

$$|V_{min}| = V_0 (1 - |\Gamma|)$$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

- Often we use the decibels (dB) to express the power levels and performance parameters
- Here we look into the the terms *return loss* and *insertion loss*

For mismatched load, the power *returned* to the generator is the **return loss**:

$$RL = -20 \log |\Gamma|(\text{dB})$$

- For passive circuits like an antenna, the return loss is always a non-negative number.

- Like reflection, we also have *transmission* coefficient
- This is useful when we have lots of elements in a transmission line.


The transmission coefficient is defined as:

$$T = 1 + \Gamma = \frac{2Z_1}{Z_0 + Z_1}$$

The **insertion loss** becomes:

$$IL = -20 \log |T| \text{dB}$$

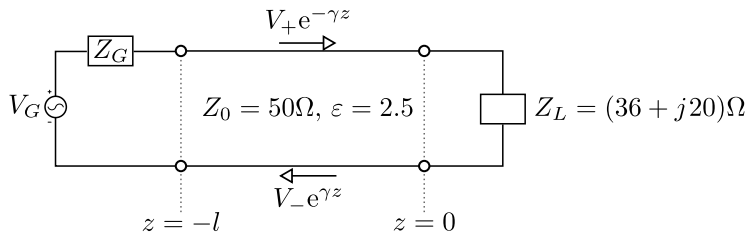We use 20 in both the definitions as we primarily are dealing with power levels.



For the TL above with a length l of 6.33 m, find the average power delivered to the load as well as the line. The source voltage is $V_G = 100\text{ V}$ operating at a frequency of 200 MHz. The source impedance Z_G is also 50Ω . First, check whether the circuit is actually a transmission line. Also find the input impedance $Z_{in} = Z(-l)$ of the line.

First, we check the electrical length of the transmission line.


$$\begin{aligned}\beta &= k = \frac{2\pi}{\lambda} = \frac{\omega}{v} \\ \Rightarrow \lambda &= \frac{v}{f} = \frac{c}{\sqrt{\epsilon_r}f} = \frac{3 \times 10^8}{\sqrt{2.5} \times 20 \times 10^6} \\ \lambda &= 10.55 \text{ m} \Rightarrow l = \frac{6.33}{10.55} = 0.6\lambda\end{aligned}$$

As $l > 0.1\lambda$, the given circuit can be treated as a transmission line.

As Z_0 is real-valued, we treat the TL as lossless.

$$\begin{aligned}Z_{in} = Z(-l) &= Z_0 \frac{Z_L + jZ_0 \tan \beta l}{Z_0 + jZ_L \tan \beta l} \\&= 50 \times \frac{(36 + j20) + j50 \tan(2\pi \times 0.6)}{50 + j(36 + j20) \tan(2\pi \times 0.6)} \\Z_{in} &= (86.15 - j10.93) \Omega\end{aligned}$$

The equivalent circuit now looks like:

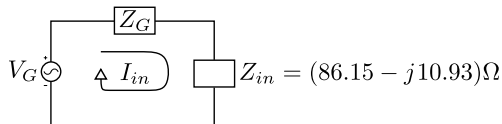

The current in the circuit is:

$$\begin{aligned}
 I_{in} &= \frac{V_G}{Z_G + Z_{in}} \\
 &= \frac{100}{50 + 86.15 - j10.93} = (0.73 + j0.06) \text{ A}
 \end{aligned}$$

The average input power is:

$$P_{in} = 1/2 \operatorname{Re}\{V_{in} I_{in}^*\} = 1/2 \operatorname{Re}\{Z_{in} I_{in} I_{in}^*\} = 23.09 \text{ W}$$

We first calculate the current $I(z)$ in the transmission line.

$$I(z) = \frac{V_+}{Z_0} \left(e^{-j\beta z} - \Gamma e^{j\beta z} \right)$$

At $z = -l$, $I(-l) = I_{in}$ and treating $\frac{V_+}{Z_0} = I_+$

$$I(-l) = I_{in} = I_+ \left(e^{+j\beta l} - \Gamma_{in} e^{-j\beta l} \right)$$

$$I_+ = I_{in} / \left(e^{+j\beta l} - \Gamma_{in} e^{-j\beta l} \right) = (-0.47 + j0.89) \text{ A}$$


The current at the load is:

$$I_L = I_+ (1 - \Gamma_L)$$

The power at the load is hence:

$$\begin{aligned} P_{load} &= 1/2 \operatorname{Re}\{I_L I_L^* Z_L\} \\ &= 23.09 \text{ W} \end{aligned}$$

THE SMITH CHART

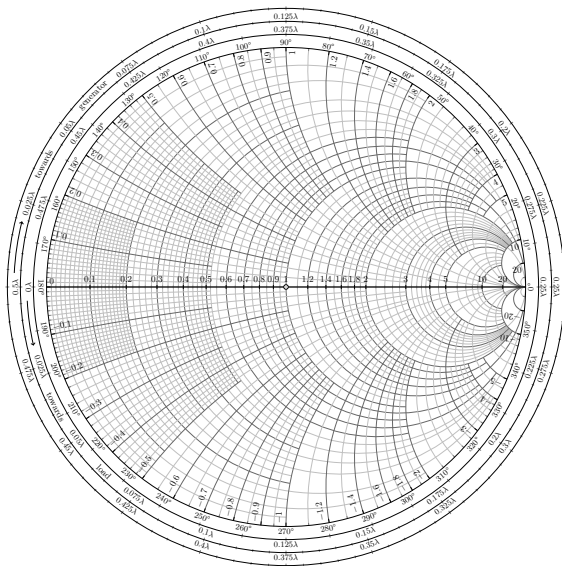

- Developed by P Smith in 1939
- To this day, it is an integral part of microwave circuit design
- Provides a tool to visualise the transmission line phenomena such as impedance matching
- It is simply a polar plot of the reflection coefficient, Γ

- In polar coordinates, $\Gamma = |\Gamma|e^{j\theta}$
- We plot the magnitude as a radius ($|\Gamma| \leq 1$) from the centre
- The angle θ ranges from -180° to 180°

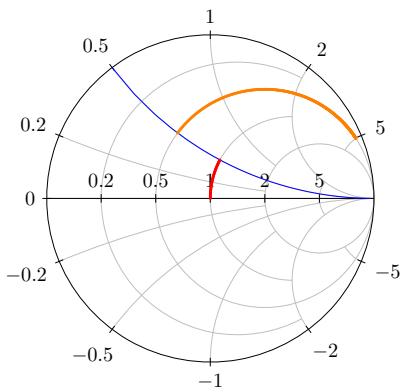


Figure 2: Γ plotted on the Smith chart