



University  
of Glasgow

# HIGH FREQUENCY COMMUNICATION SYSTEMS

## Lecture 5

---


Hasan T Abbas & Qammer H Abbasi

Spring 2021

- The Smith Chart
- The Magic of Quarter-wave Transformer
- Load matching through stubs


SMITH CHART

---

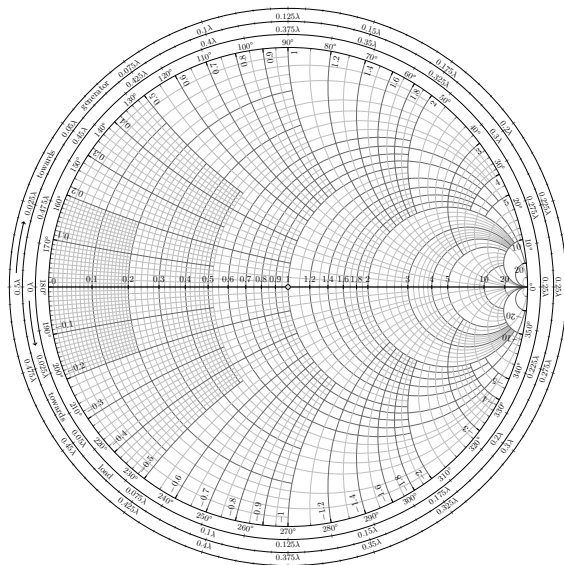

- Developed by P Smith in 1939
- To this day, it is an integral part of microwave circuit design
- Provides a tool to visualise the transmission line phenomena such as impedance matching
- It is simply a polar plot of the reflection coefficient,  $\Gamma$

- In polar coordinates,  $\Gamma = |\Gamma|e^{j\theta}$
- We plot the magnitude as a radius ( $|\Gamma| \leq 1$ ) from the centre
- The angle  $\theta$  ranges from  $-180^\circ$  to  $180^\circ$
- **The origin** or the centre of the Smith chart is the ideal, matched point.

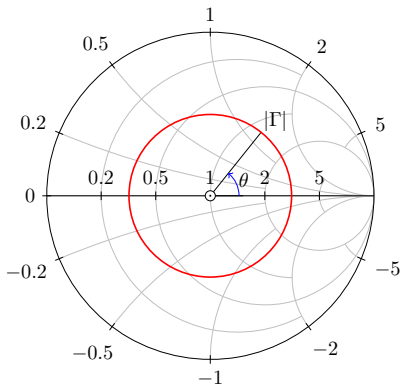

For lossless TLs, the *normalised* load impedance at  $l = 0$  is a complex number:

$$z_L = \frac{Z_L}{Z_0} = \frac{1 + |\Gamma|e^{j\theta}}{1 - |\Gamma|e^{j\theta}}$$

Treating  $\Gamma = \Gamma_r + j\Gamma_i$ , the real and imaginary parts of  $z_L$  are:

$$r_L = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$

$$x_L = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}$$


which can be written as two equations of circles:

$$\left(\Gamma_r - \frac{r_L}{1 + r_L}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1 + r_L}\right)^2 \quad \text{(Resistance Circle)}$$

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x_L}\right)^2 = \left(\frac{1}{x_L}\right)^2 \quad \text{(Reactance Circle)}$$

- Lets look at some examples
  - Taking  $r_L = 1$  and lets plot in the  $\Gamma_r, \Gamma_i$  plane
  - But first, the equation for the resistance circle is:

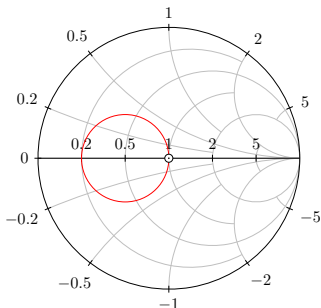
$$\left(\Gamma_r - \frac{1}{1+1}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+1}\right)^2$$






- Now the reactance circle where we take  $z_L = j1 \implies x_L = 1$
- The reactance circle equation becomes:

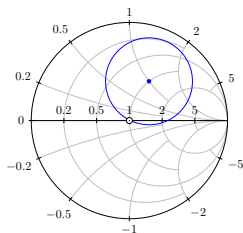
$$(\Gamma_r - 1)^2 + (\Gamma_i - 1)^2 = 1$$



The top half is the *inductive* region and the bottom half is the *capacitive* region.

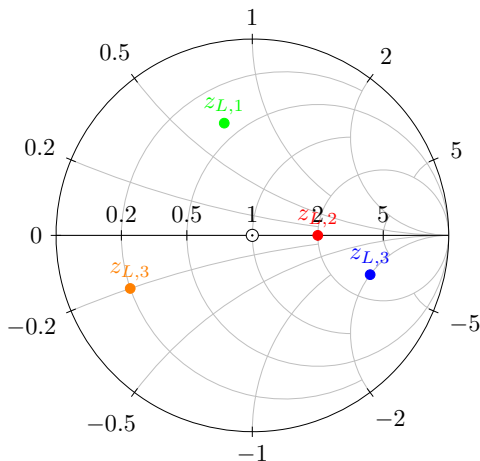
- We normally normalise the impedance to  $50\ \Omega$ .
- However, the chart can be used for any value.
- $z_{L,1} = 0.4 + j0.7$
- $z_{L,2} = 2$
- $z_{L,3} = 3 - j2$
- $z_{L,4} = 0.2 - j0.2$



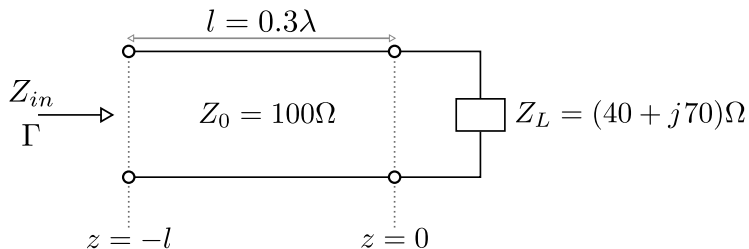


- Lets find the input impedance  $Z_{in} = Z(-l)$  of the line.
- Also the reflection coefficient,  $\Gamma$  and the VSWR

# EXAMPLE - FINDING THE INPUT IMPEDANCE

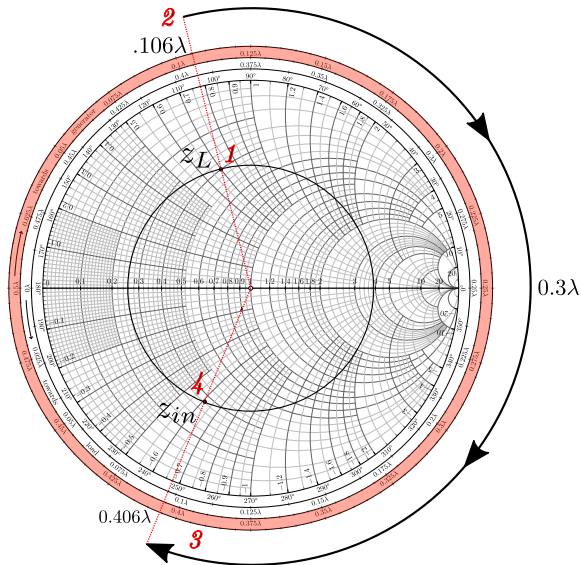


- From the Smith chart, we first plot the normalised load impedance  $z_L$
- We then draw a circle centred on the origin with a radius such that  $z_L$  lies on the circle
- Draw a line from the origin passing through  $z_L$  to the outer circle of the Smith chart
- Move  $l = 0.3\lambda$  towards the generator
- Draw a line from the origin to the new rotated point.
- The intersection point with the circle and the line drawn gives us the normalised input impedance  $z_{in} \approx 0.365 - j0.61$ .

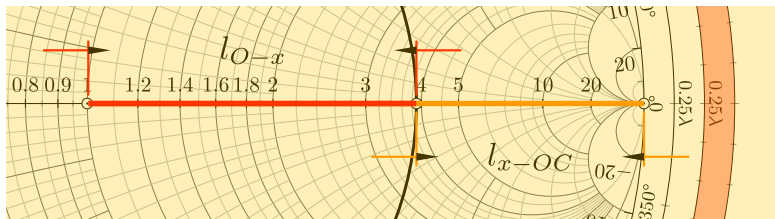


- The ratio of the length of the line segments  $l_{O-x}$  and  $l_{O-OC}$  gives us VSWR
- The point on the right of the Smith chart is the open-circuit point ( $r = \infty, x = \infty$ )
- For this example, we get  $VSWR \approx 3.9$ .
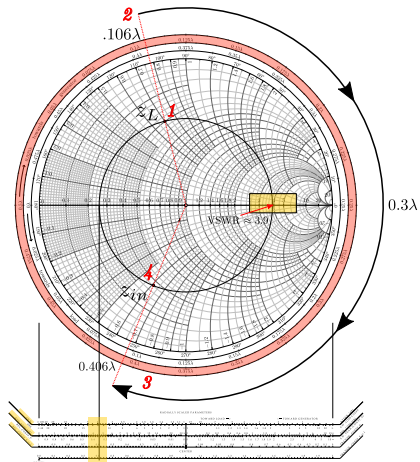
## FINDING THE VSWR - USING THE RADIALLY SCALED PARAMETERS



- Some Smith charts provide radially scaled parameters at the bottom of the sheet.
- By drawing a vertical line from the left of the circle to the bottom,


## USING THE RADIAL AXIS PARAMETERS

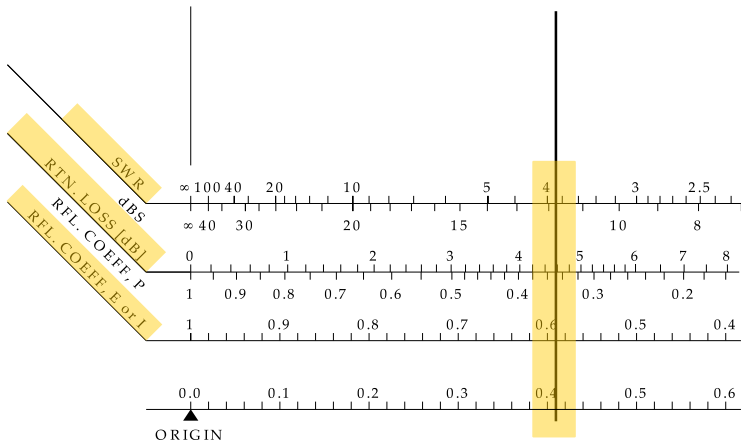


- Reading from the scales, we get,  $VSWR \approx 3.9$ ,  $|\Gamma| \approx .59$ , and the return loss  $\approx 4.600$  dB



- The ratio of the length of the line segments  $l_{O-x}$  and  $l_{O-SC}$  gives us  $|\Gamma|$
- The point on the left of the Smith chart is the short-circuit point ( $r = 0, x = 0$ )

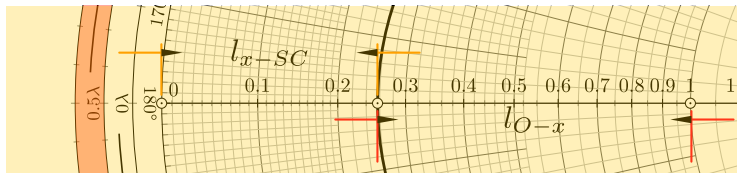


- Admittance is just the reciprocal of the impedance
- On the Smith chart, it represents the diametrically opposite point on the  $|\Gamma|$ -circle
- For  $z_L = 0.4 + j0.7$ ,  
 $y_L = 1/z_L = 0.6 - j1.08$
- Alternatively, we can use an admittance Smith chart

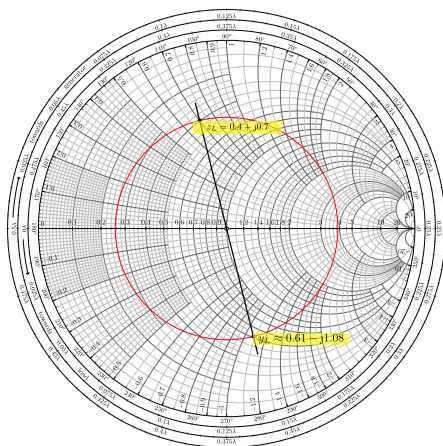

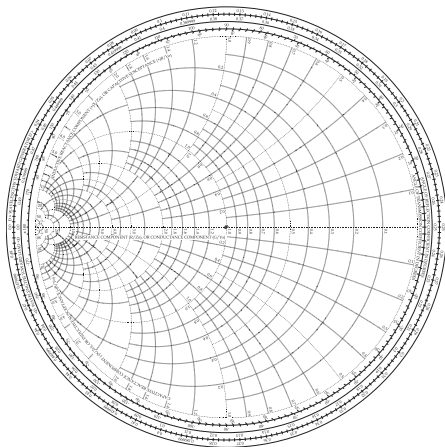
## STUB MATCHING

---


- Stub matching introduces additional impedances/admittances in the line (often in parallel)
- As parallel *admittances* are added up, it is convenient to use a Smith chart showing admittance rather than impedance.
- The result is a horizontally flipped admittance Smith chart.



- A short circuit stub of length  $l$  is introduced in *parallel* at distance  $d$  from the load
- As seen in the figure, we need the input impedance of the parallel combination to be  $Z_0$  at the point A-A'
- In other words,  $y_s + y_A = y_{in} = 1$
- As we are using a short circuit stub,  $y_s = -jb_A$
- The objective is to find the lengths  $d$  and  $l$  that generate a unity real part and zero imaginary part of admittance respectively.

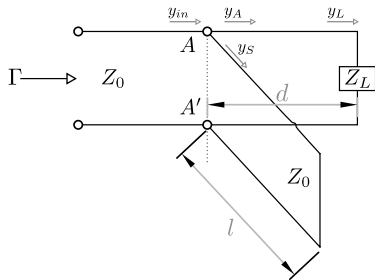


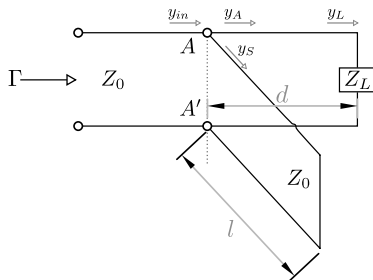- For a  $50\ \Omega$  transmission line connected to a load impedance  $Z_L = (35 - j45.50)\ \Omega$
- Find the position and length of the short circuit stub that matches the load to the line.
- $z_L$  becomes  $0.70 - j0.95$




1. Draw  $z_L$  and draw the  $|\Gamma|$ -circle
2. Find  $y_L$  using a diametrically opposite line
3. Extend the line to the perimeter and note down the *wavelengths toward generator* value
4. Plot the  $g = 1$  circle and note down the two points of intersection  $y_{A,1} = 1 + jb_{A,1}$  and  $y_{A,2} = 1 + jb_{A,2}$ .
5. Find the distances  $d_1$  and  $d_2$  from the generator for the two points above
6. Find the lengths  $l_1$  and  $l_2$  to get the admittances  $-jb_{A,1}$  and  $-jb_{A,2}$
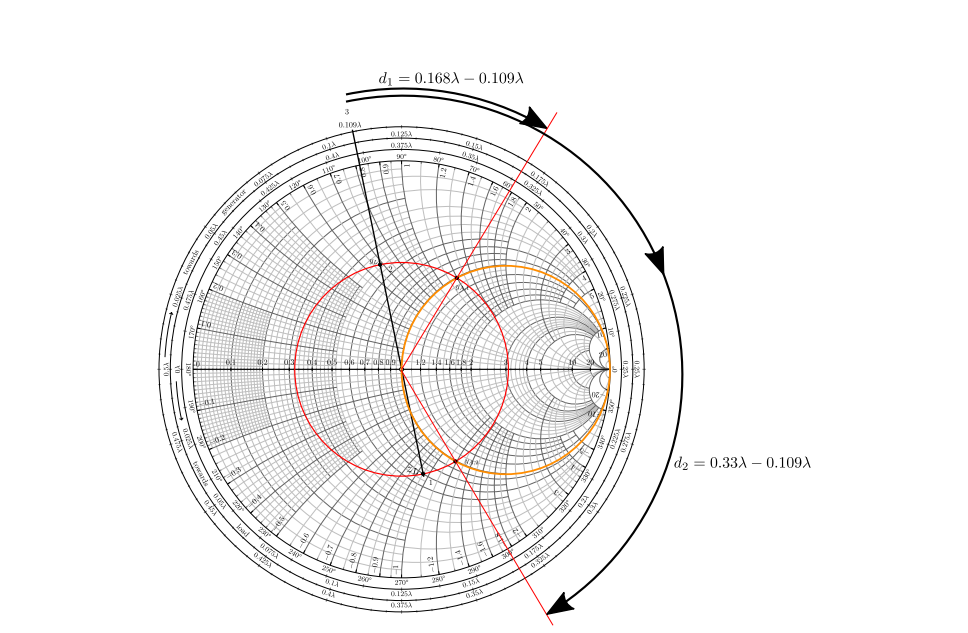
## FINDING THE STUB DISTANCE FROM THE LOAD







# FINDING THE STUB LENGTH FROM THE LOAD

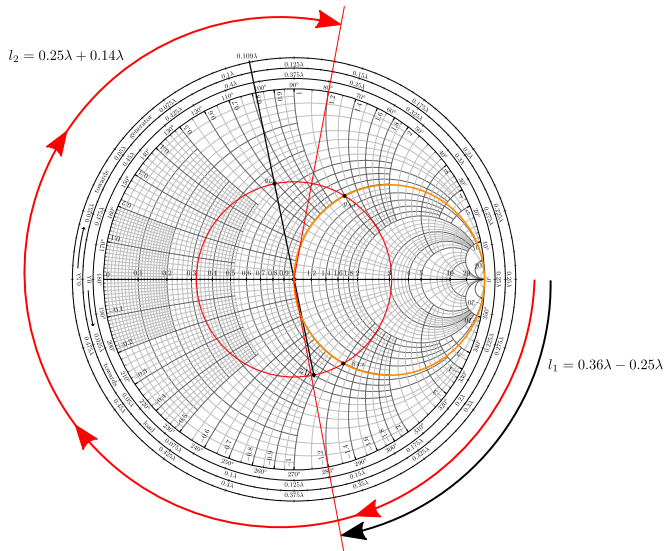

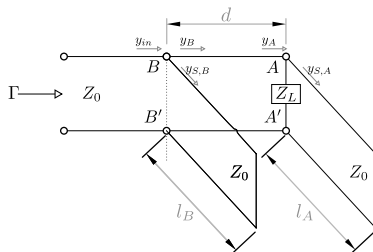- Single stub matching requires a precise placement of the stub from the load
  - This distance is a function of frequency and therefore, changes if the source frequency is changed
  - Also, we can't engineer the length of the stub of any given value
- To avoid this and use matching at more than one frequency, we use double stub matching




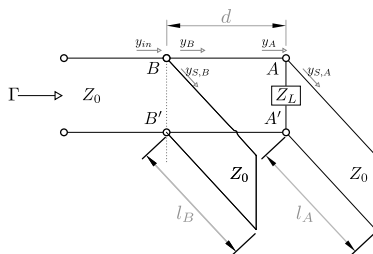- For a  $50\ \Omega$  transmission line connected to a load impedance  $Z_L = (60 + j80)\ \Omega$
- A double-stub tuner spaced  $d = \lambda/8$  distance from the load for matching.
- Find the lengths of the short circuit stubs that match the load to the line.
- $z_L$  becomes  $1.2 + j1.6$
- $y_L$  becomes  $0.3 - j0.40$



1. Plot the  $g = 1$ -circle
2. Rotate the above circle by  $\lambda/8$  towards the load
3. Plot  $y_L = 0.3 - j0.40$  and draw the  $g = 0.3$ -circle
4. Mark the points  $y_{A,1} = 0.30 + j0.30$  and  $y_{A,2} = 0.30 + j1.75$  that are points of intersection between the  $g = 0.3$ -circle and rotated  $g = 1$ -circle
5. The corresponding points on the  $g = 1$ -circle are  $y_{B,1} = 1 + j1.40$  and  $y_{B,2} = 1 - j3.50$ .

## FINDING THE IMPEDANCES

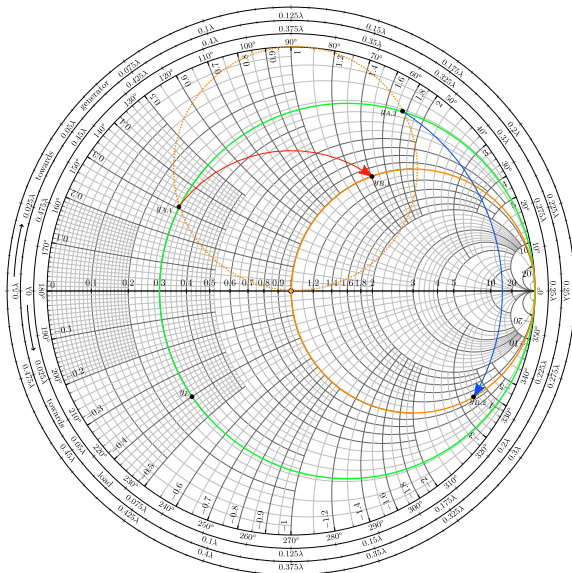

- At the load ( $A - A'$ ), the admittance is  $y_A = y_L + y_{S,A}$
- The admittances of the stub are
$$y_{A,1} - y_L = 0.3 + j0.30 - (0.30 - j0.40) = j0.70 \text{ and}$$
$$y_{A,2} - y_L = 0.30 + j1.75 - (0.30 - j0.40) = j2.15$$
- Similarly, the admittances are simply the conjugate of  $y_B$
- They are  $y_{B,1} = -j1.40$  and  $y_{B,2} = -j3.50$
- The lengths of the stub can be found in the same manner as we did for the single stub.